



EE323

MIDTERM

October 23, 2001  
1:30pm - 3:00pm

Open books, open notes. Answer all questions.  
Use the other side of the paper if you require more space.  
Total mark: 50

Name: Solution

Stud. #: \_\_\_\_\_

1. Question 1 (15 marks)


In the non-inverting voltage-to-current converter shown, the basic op-amp has infinite input resistance and zero output resistance. For input  $v_s$  and output  $i_o$ , find an expression for the feedback factor  $\beta = v_f/i_o$ . For an open loop gain  $A = 10^3$  mA/V, what must  $\beta$  be for a closed-loop gain of 10 mA/V? For this  $\beta$ , find values of  $R_1$ ,  $R_2$ , and  $r$  to make  $i_o/v_s = 10$  mA/V, (while allowing the voltage across  $R_L$  to be as large as possible for a given power supply, yet using no resistor smaller than  $150\Omega$ ). What is the value of  $i_o$  when  $v_s = 1$  V?

(\*)

$$i_2 = i_o \frac{r}{r+R_1+R_2}$$

$$v_f = i_2 R_1 = \frac{r R_1}{r+R_1+R_2} i_o$$
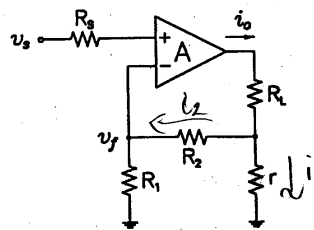
$$\beta = \frac{v_f}{i_o} = \frac{r R_1}{r+R_1+R_2}$$



(\*)  $A_{OL} = 10^3 \text{ mA/V}$  }  $A_{CL} = \frac{A_{OL}}{1+A_{OL}\beta}$  or  $\beta \approx \frac{1}{A_{CL}} = \frac{1}{10 \text{ mA/V}} = \boxed{100 \frac{\text{V}}{\text{A}}}$  (99-6% he exact)


$A_{CL} = 10 \text{ mA/V}$

(\*) Choose  $r = 150\Omega$ ,  $R_2 = 150\Omega \Rightarrow 100 = \frac{150 R_1}{300 + R_1}$  or  $50 R_1 = 30000$   
 $R_1 = \underline{\underline{600\Omega}}$

(\*)  $i_o = A_{CL} v_s = \left(10 \frac{\text{mA}}{\text{V}}\right) (1 \text{ V}) = \underline{\underline{10 \text{ mA}}}$
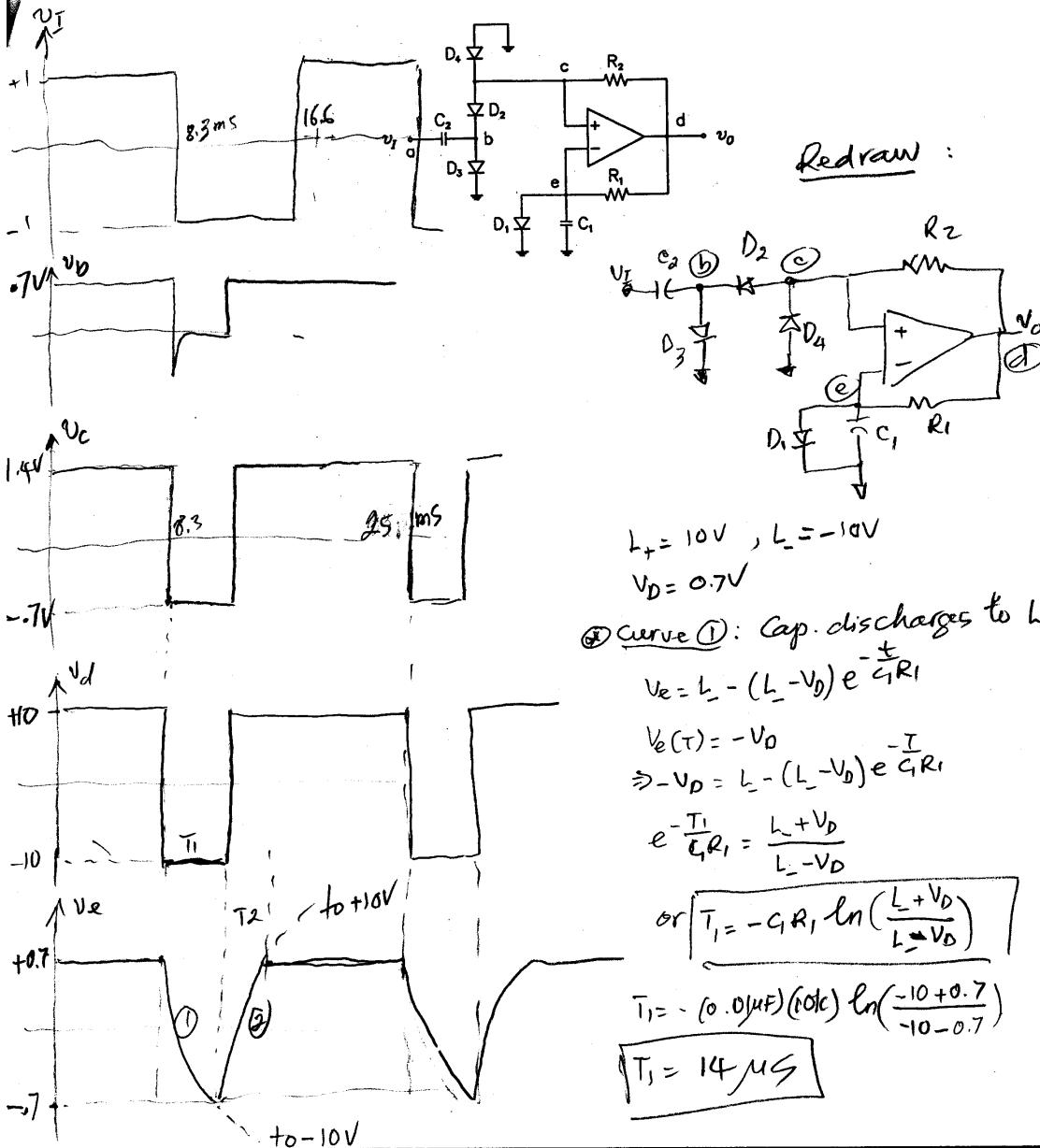
## 2. Question 2 (20 marks)

Consider the circuit shown, using diodes which conduct at  $V_D = 0.7V$ , and an amplifier saturating at  $\pm 10V$ , with  $R_1 = R_2 = 10\text{ K}$  and  $C_1 = 10C_2 = 0.01\text{ }\mu\text{F}$ . Find the output pulse width and frequency, if  $v_i$  is a 60 Hz square wave of 2Vpp amplitude. Sketch the waveforms at nodes a through e. What is the smallest input signal required to trigger the circuit? How long does it take for this circuit to be ready for a new input?



④ Curve 2: Cap. charges to  $L_+$

Same  $T_1 = T_2$  since discharges from  $+0.7V$  to  $-0.7V$   
and charges from  $-0.7V$  to  $+0.7V$

$$\therefore \underline{T_2 = 14 \mu s} \text{ (recovering period)}$$

The circuit is ready for the next trigger signal  
(negative edge) at  $8.3ms + \underline{28 \mu s} = 8.33ms$  (the next  
negative edge for  $60Hz$  input is at  $25ms$ )

④ The output has a period of  $25ms - 8.3ms = 16.7ms$


$$f = \frac{1}{T} = \frac{1}{16.7ms} = \underline{60Hz}$$

(note that duty cycle is not 50% as  $V_{IN}$ )

④ The smallest input signal requires is  $1.4V_{pp}$ .
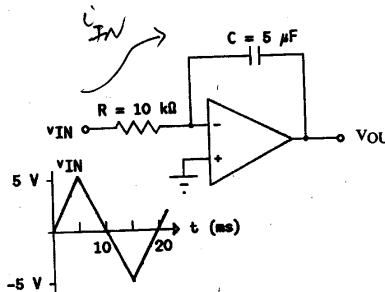
### 3. Question 3 (15 marks)

A 5V peak triangular voltage with a period of 20ms, depicted on the axis shown below, is applied to an ideal op-amp integrator. Sketch  $v_{OUT}$  as a function of time. The capacitor has zero initial charge.



$$i_N = \frac{v_{IN}}{R}$$

$$v_C = v_O$$

$$i_N = C \frac{dv_C}{dt} = -\frac{v_{IN}}{R}$$

$$\frac{dv_C}{dt} = -\frac{1}{RC} v_{IN}$$

$$v_O = v_C = -\frac{1}{RC} \int_0^t v_{IN} dt$$

①  $0 < t < 5 \text{ ms}$ ,  $v_{IN} = \alpha t$  where  $\alpha = \frac{1 \text{ V}}{\text{ms}}$  and  $t$  is in ms

$$RC = (10 \text{ k}\Omega)(5 \mu\text{F}) = 50 \text{ ms}$$

$$\Rightarrow v_O = -\frac{1}{RC} \int_0^t \alpha t dt = -\frac{\alpha t^2}{2RC} = -\frac{1 \text{ V/ms}}{2(50 \text{ ms})} t^2 = -\frac{t^2}{100 \text{ ms}^2} \text{ V}$$

$$\left. \begin{array}{l} t=0, v_O=0 \\ t=5 \text{ ms}, v_O = -\frac{(5 \text{ ms})^2}{100 \text{ ms}^2} = -0.25 \text{ V} \end{array} \right\} \text{ parabola}$$

②  $5 < t < 10 \text{ ms} \Rightarrow v_{IN}$  positive (but returning to zero),  $v_O$  will continue increasing negatively but its slope will become more shallow as time progresses  $t=10 \text{ ms} \Rightarrow v_O = -0.5 \text{ V}$

③ Over the next 10 ms, during which time  $v_{IN}$  become negative,  $v_O$  will begin to increase from the negative peak, reaching zero at  $t = 20 \text{ ms}$ .

